


trr Measurements at High di/dt

Preliminary Discussion

Discussion

- An attempt was made to determine how MOSFETs' diodes behave at high di/dt such as found in a synchronous buck circuit
- This is an attempt to myth-bust statements such as:
 - Schottkies have extremely low t_{rr} and should be used in parallel with MOSFETs to reduce losses
 - Q_{rr} is constant, $I_{rr} \times t_{rr} = \text{constant}$
 - t_{rr} losses are not significant

Tester Schematic

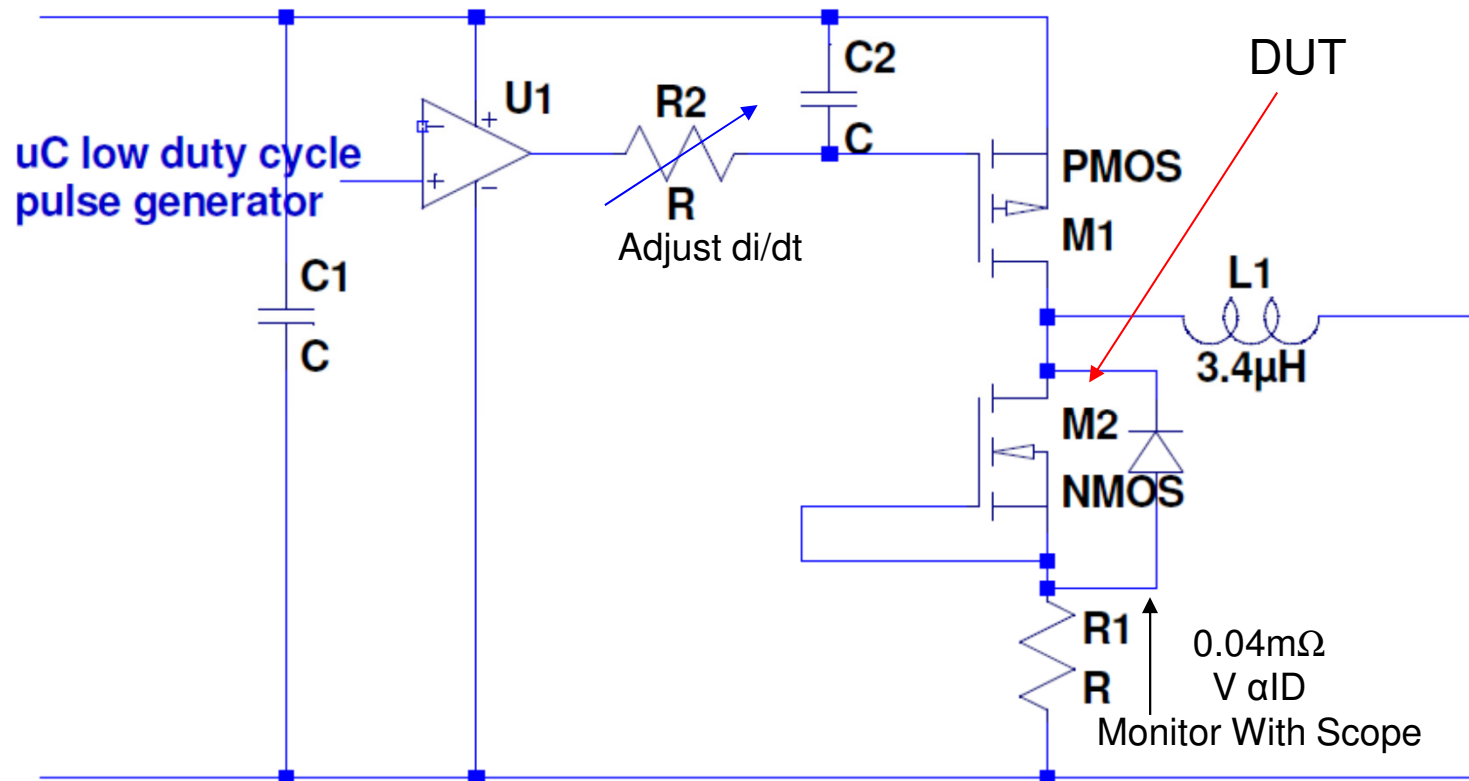


Testing Conditions

- AM7436N MOSFET
- $V_{IN} = 12V$
- $I_F = 10A$
- Sense resistor = 40m Ohm
- All time measurements are for t_a only, ignore t_b
 - $t_a \gg t_b$
 - Losses for $t_b \sim 0$ as V_{DS} of diode has ramped up



Traditional Conditions: 100A/us

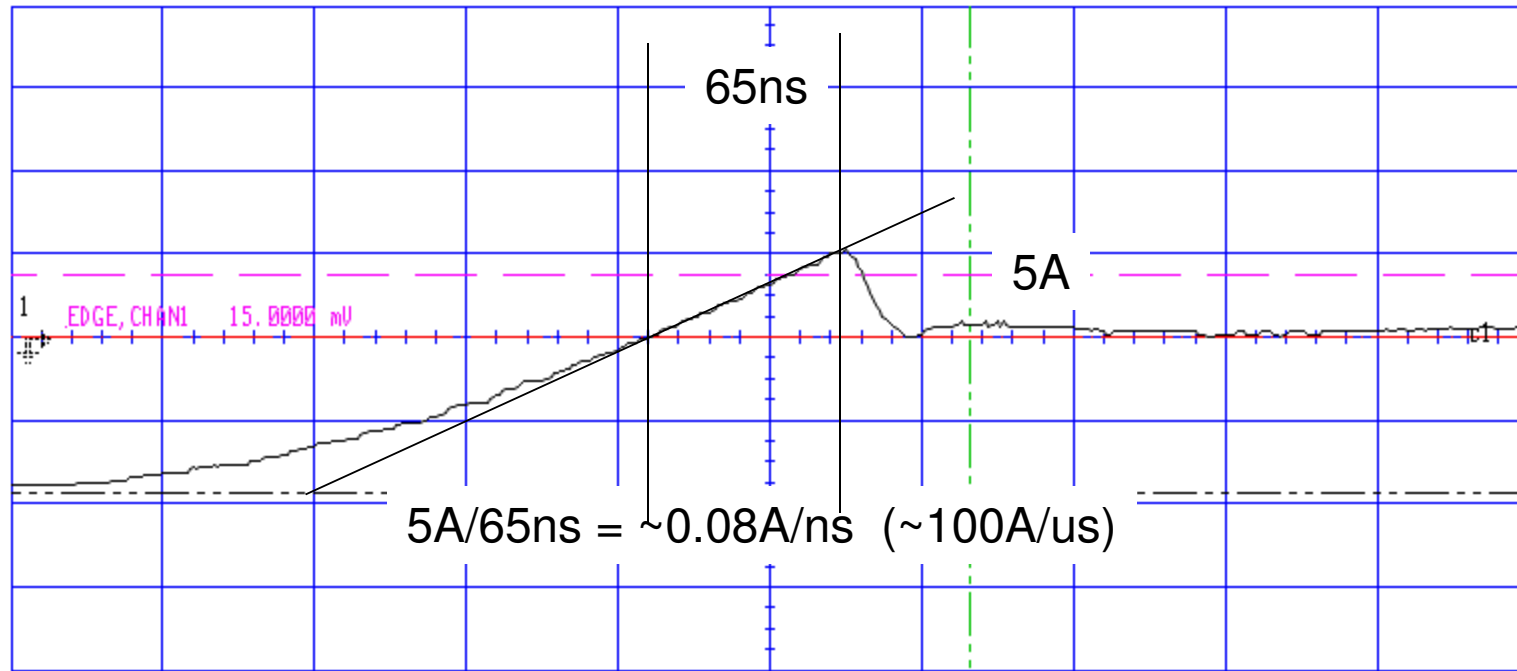-276.000 ns Main: 50.0 ns/div CENTER -26.000 ns REALTIME 224.000 ns
 -276.000 ns 50.0 ns/div -26.000 ns SINGLE 224.000 ns




	Sensitivity	Offset	Probe	Coupling	Impedance	Markers
Channel 1	200 mV/div	0.00000 V	10:1	dc	1M ohm	Y2marker(c1) = 0.00000 V Y1marker(c1) = -375.000 mV




2A/ns

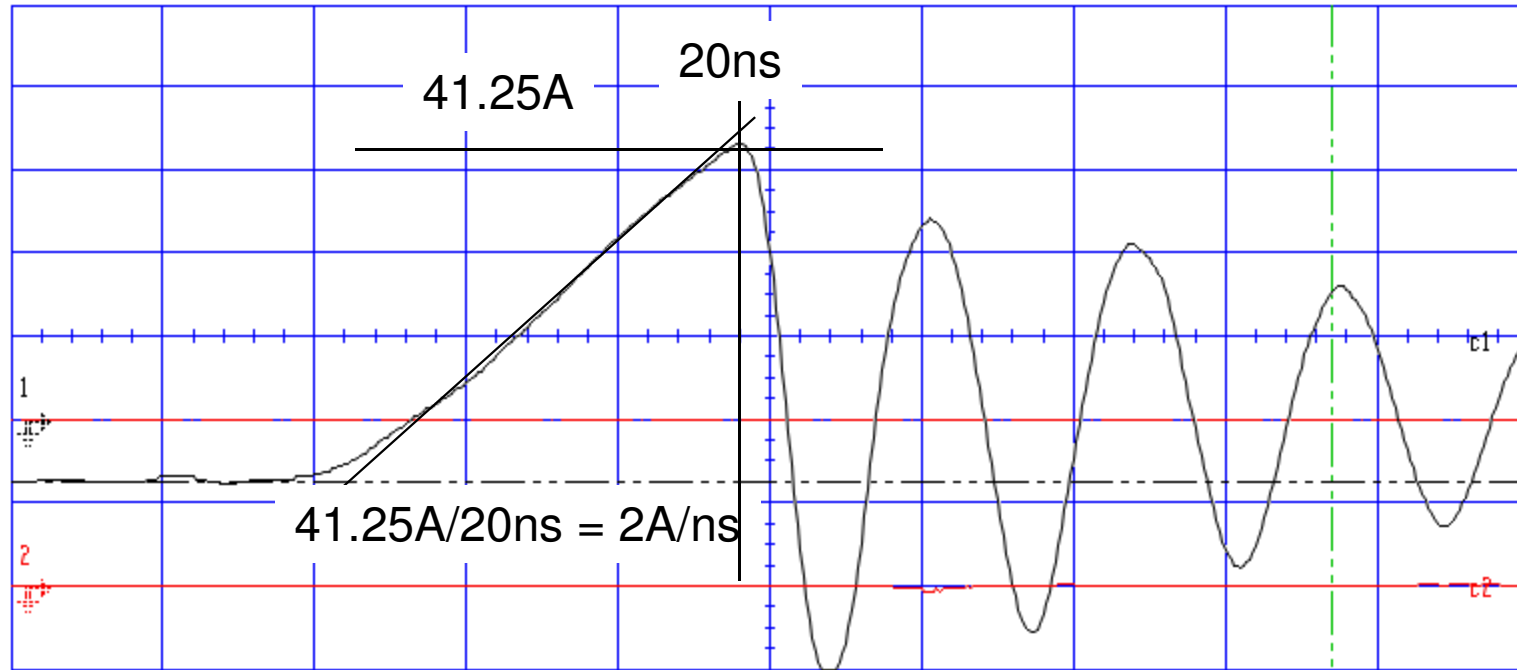-47.000 ns Main: 10.0 ns/div CENTER 3.000 ns REALTIME 53.000 ns
 -47.000 ns 10.0 ns/div 3.000 ns SINGLE 53.000 ns



	Sensitivity	Offset	Probe	Coupling	Impedance	Markers
Channel 1	500 mV/div	500.000 mV	10:1	dc	1M ohm	Y2marker(c1) = 0.00000 V
Channel 2	5.00 V/div	15.0000 V	10:1	dc	1M ohm	Y1marker(c1) = -375.000 mV

5A/ns

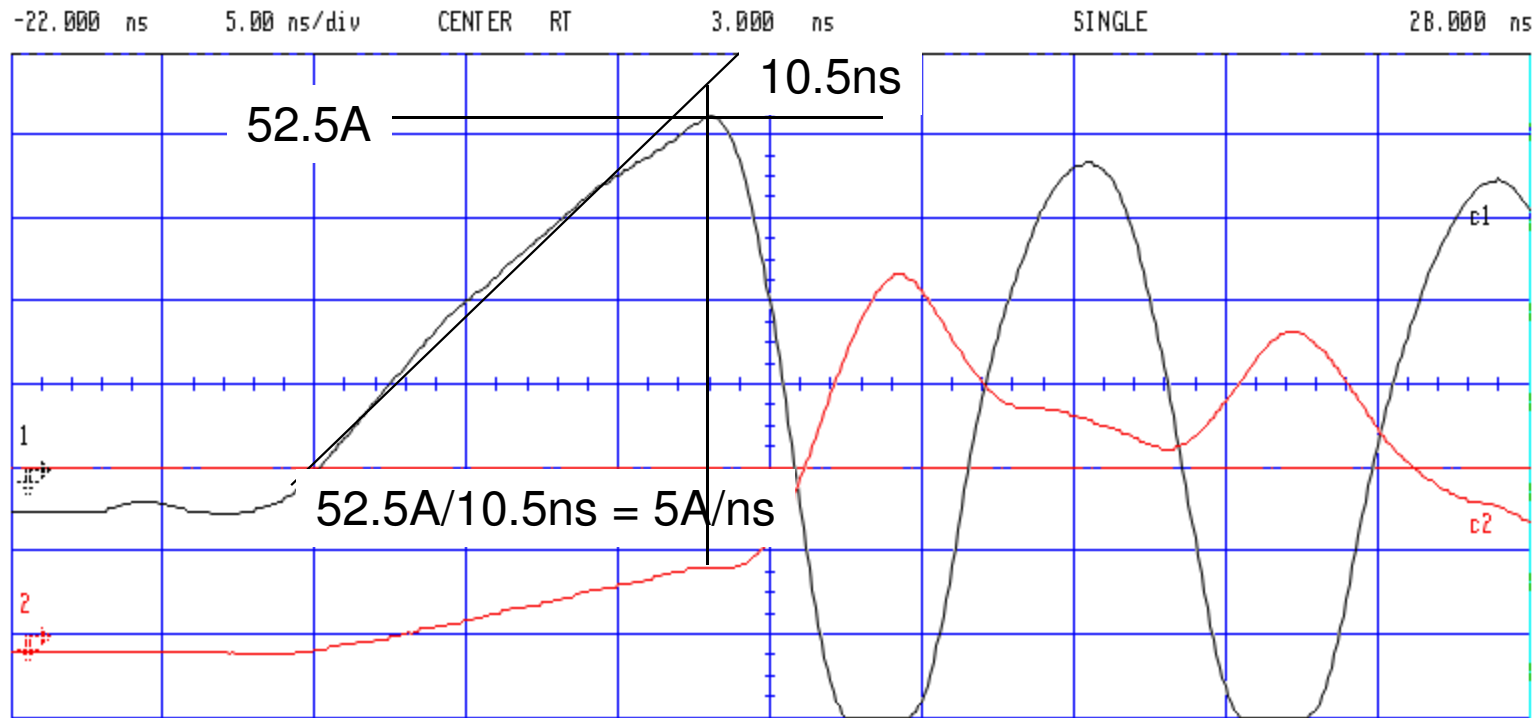

	Sensitivity	Offset	Probe	Coupling	Impedance	Markers
Channel 1	500 mV/div	500.000 mV	10:1	dc	1M ohm	Y2marker(c1) = 0.00000 V
Channel 2	5.00 V/div	15.0000 V	10:1	dc	1M ohm	Y1marker(c1) = 6.75000 V



Results

Di/Dt A/ns	Irr peak A	trr ns	trr * di/dt	Qrr nC
0.1	5	65		160
2	41	20	40	410
5	52	10.5	50	275

Conclusions

This data needs verification, however we make the following assumptions:

- Q_{rr} at $>1A/ns \gg$ at $di/dt = 100A/us$. The reason for the increase is probably natural recombination over time at slower di/dt
- The data show Q_{rr} decreasing from $2A/ns$ to $5A/ns$, this is not likely the case for a perfect circuit. We think IRR is being capped by other parts of the circuit, i.e. parasitics and circuit resistance play, but this is how a real circuit will behave and di/dt of $>5A/ns$ is quite possible so maybe at high di/dt t_{rr} is less important and parasitics play a part
- $t_{rr} \times di/dt = \sim \text{constant}$ at high di/dt
- The data actually shows significant +ve VDS during t_a . This was a surprise, but some +ve VDS is likely due to substrate and package resistance at these high currents.
- We will design new board and see if data makes any more sense, more data points are needed.
 - More: see next page

Other Conclusions/Findings

- Schottkies have finite trr too. Many Schottkies are no better than PN diodes
 - MOSFETs with schottkies have quite long trr
 - Conditions for some Schottky trr are unreasonably low current as at higher currents PN junction comes into play
- This experiment would suggest trr losses are a significant cause of losses in the top FET, but maybe not quite as much as expected due to:
 - +VE VDS during recovery (although this may be losses in the bottom FET)
 - Irr being limited by other circuit components
 - Very high di/dt does reduce losses and trr < 10ns is possible